



# Google AI Quantum

## Superconducting Integrated Circuits for QC

Ofer Naaman

Workshop on Cryogenic Electronics

Fermi National Lab 6/20/19



# Near Term Gaps

- Wiring
- Signal integrity
- Passives
- Amplifiers


# Long Term Solutions

- Reduce I/O
- Cryogenic control - CMOS and SC
- Superconducting  $\mu$ wave components




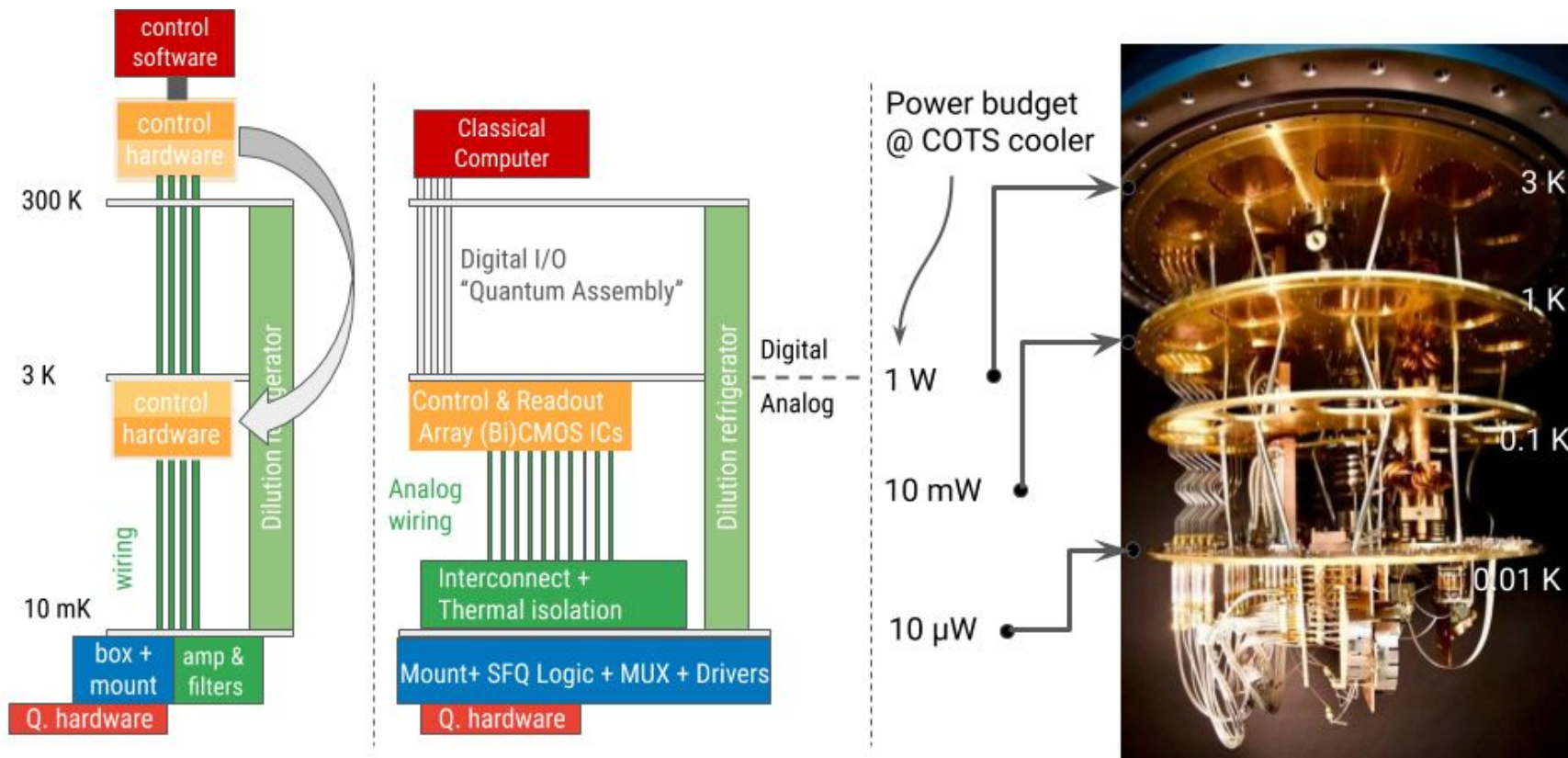
# Scale by Integrating Control Electronics



# Agenda

- Aspects of superconducting IC design
  - Lossless wiring
  - Active devices - Josephson junctions
- Design examples
  - Microwave switches
  - Mixers and modulators
  - Amplifiers and circulators



# Aspects of Superconducting IC Design




# Superconductors are Lossless

Implication:

- Can use long, sub-micron wiring (eg. spiral inductor) at microwave frequencies.
- Compact transmission-line resonators with  $Q > 1M$

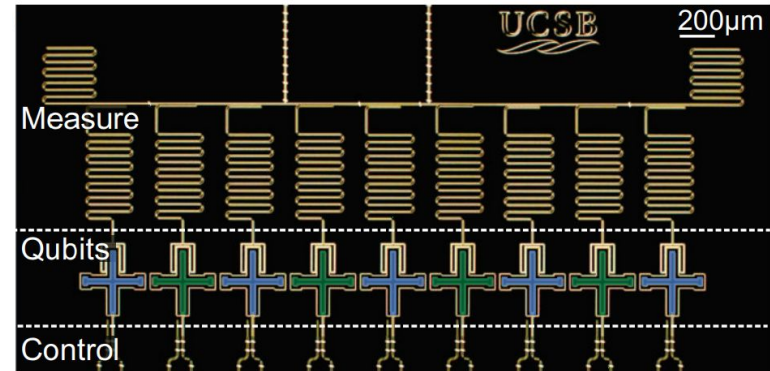But: watch for high Q parasitic resonances!




# Superconductors are Lossless

Implication:

- Transformers work at DC

$$\begin{array}{c} \mathbf{V} = -i\omega\hat{L}\mathbf{I} \\ \Downarrow \\ \Phi = \hat{L}\mathbf{I} \end{array}$$

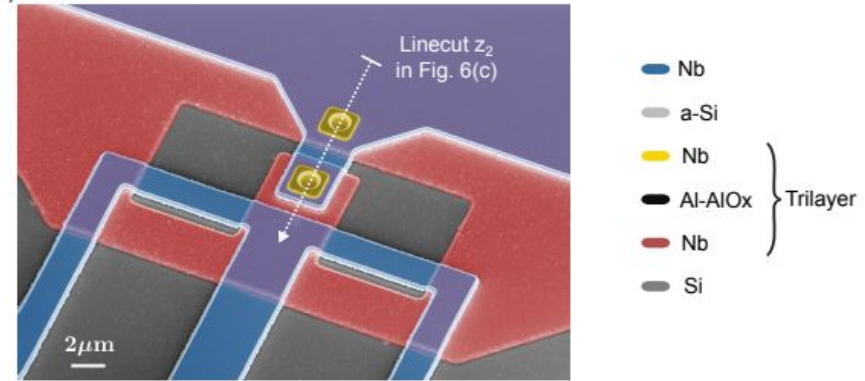where  $\Phi$  is the flux  $\Phi = \int V dt$



NIST- F. Lecocq, Phys. Rev. Applied (2017)

But:

- Stray magnetic fields generate DC current as well
- Every SC loop can trap flux




# Active Devices: Josephson Junctions

- Tunnel junction between superconductors
- Critical current  $I_c \propto \text{area}$ 
  - 10's nA -  $\mu\text{A}$  in qubit circuits
  - $\mu\text{A}$  - 100's  $\mu\text{A}$  in microwave and logic circuits


- When  $I < I_c$  : lossless nonlinear inductor

$$L_J = \frac{\hbar}{2eI_c \cos \delta}, \quad \delta = \sin^{-1}(I/I_c) \quad 1\mu\text{A} \rightarrow 329 \text{ pH}$$

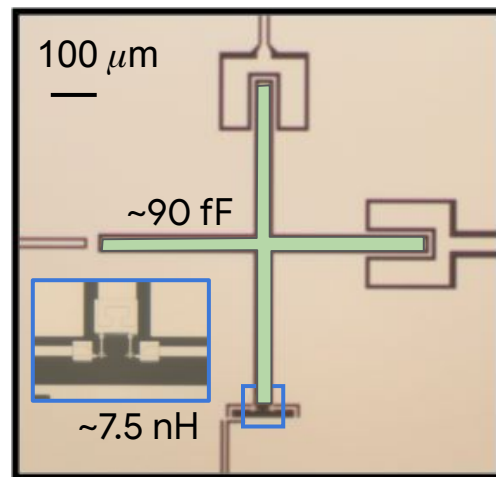- Inductance is tunable if we control the current
  - Two junctions in parallel: DC SQUID
  - One junction in parallel with inductor: RF SQUID



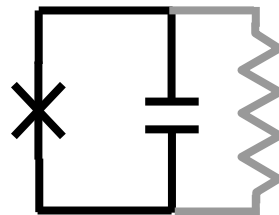Lots of lossless inductance in small space






# Active Devices: Josephson Junctions

- Tunnel junction between superconductors
- Critical current  $I_c \propto \text{area}$ 
  - 10's nA -  $\mu\text{A}$  in qubit circuits
  - $\mu\text{A}$  - 100's  $\mu\text{A}$  in microwave and logic circuits


- When  $I < I_c$  : lossless nonlinear inductor

$$L_J = \frac{\hbar}{2eI_c \cos \delta}, \quad \delta = \sin^{-1}(I/I_c) \quad 1\mu\text{A} \rightarrow 329 \text{ pH}$$

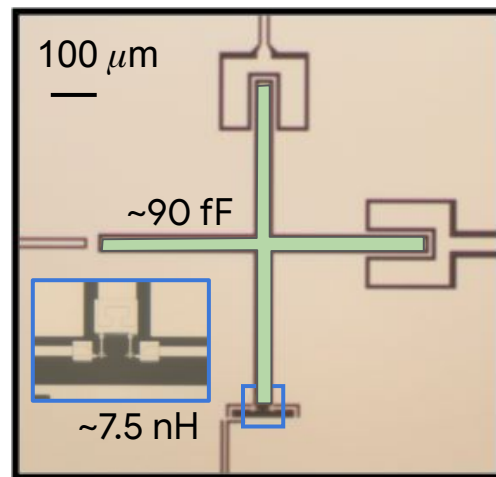- Inductance is tunable if we control the current
  - Two junctions in parallel: DC SQUID
  - One junction in parallel with inductor: RF SQUID





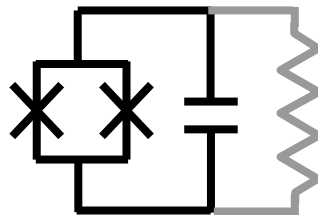Lots of lossless inductance in small space


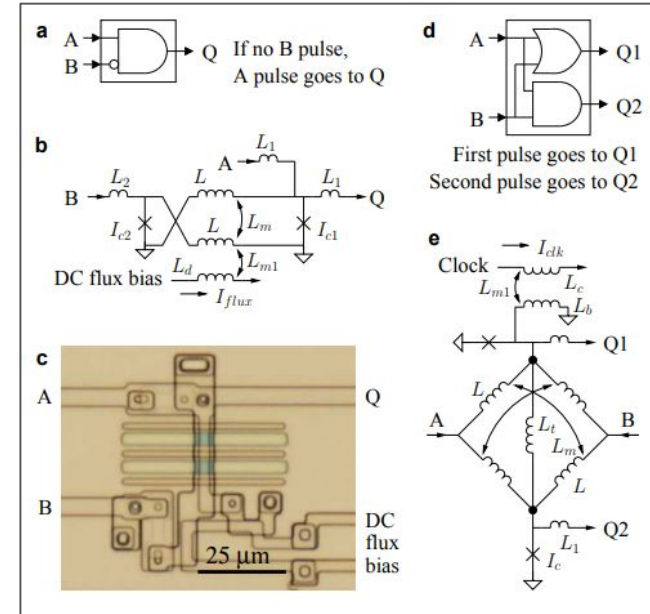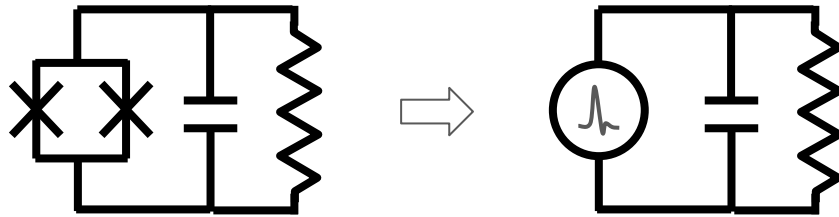
# Active Devices: Josephson Junctions

- Tunnel junction between superconductors
- Critical current  $I_c \propto \text{area}$ 
  - 10's nA -  $\mu\text{A}$  in qubit circuits
  - $\mu\text{A}$  - 100's  $\mu\text{A}$  in microwave and logic circuits
- When  $I > I_c$ :
  - dissipative current through shunt resistance
  - JJ is a pulsed voltage source - used for SFQ logic
  - SFQ pulse area  $2\text{mV} \times 1\text{ps}$  - fast and quantum accurate



Herr, J. Appl. Phys. (2011)


More on digital and SFQ - later today



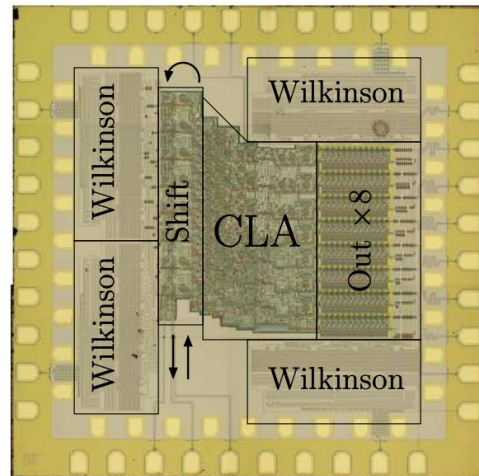
# Scaling of SFQ Circuits for mK Integration

- Power:
  - SFQ junctions are typically critically damped
  - $I_c \sim 100 \mu\text{A}$
  - Energy dissipated  $\sim \Phi_0 I_c f_{\text{clk}} \sim 0.2 \text{ nW per JJ at } 10 \text{ GHz}$
- Size:
  - SFQ tech works at fixed  $L I_c \sim \text{few flux quanta}$
  - Maximum reliable  $I_c$  density  $\sim 20 \text{ kA/cm}^2$
- Scaling:
  - Allow fixed power density
  - High  $I_c$ : integration limited by max power
  - Low  $I_c$ : integration limited by inductor size

8b CLA ca. 2011  
Northrop (RQL)  
~800 JJ



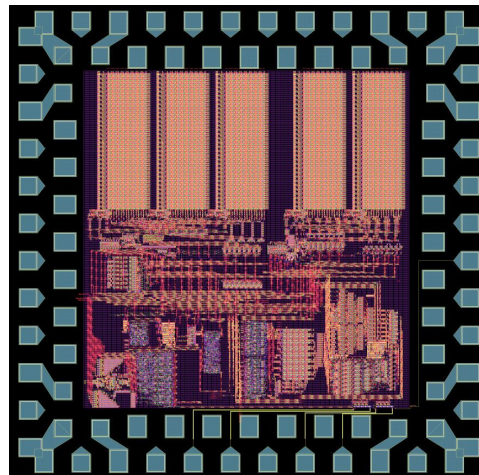8b CPU ca. 2016  
Northrop (RQL)  
~17k JJ



# Challenges in Superconductor Circuit Design

- Advantages

- compact passives
- Low loss
- Low power dissipation
- SFQ pulses - fast and accurate

- Challenges

- No tunable open circuit
- Typically low impedance to GND
- Poor isolation, e.g. connecting to bus
- Low power handling
- Flux trapping
- Foundries

	Semiconductor	Superconductor
<b>Wiring</b>	R, C	L, C (transmission lines)
<b>Traps</b>	Charge	Charge + Flux
<b>Voltage / Current</b>	volt, milliamp	microvolt, microamp
<b>Parasitic</b>	skin effect	kinetic inductance
<b>Active device</b>	$R_{ON}$ to open circuit, high Z gate	Inductive, no open circuit, low Z gate



# Superconducting IC Design Examples







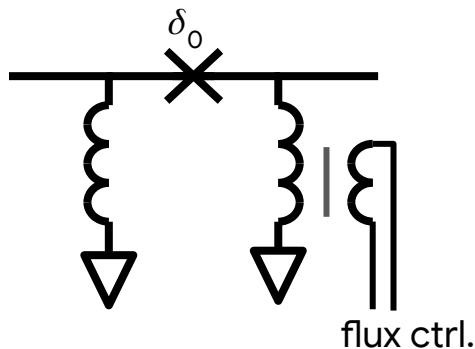
# Microwave Switches for QC – Signal Routing

How to implement a microwave switch?

- We don't have a good switchable “open circuit”
- No power dissipation on chip
- Low insertion loss and wide-band



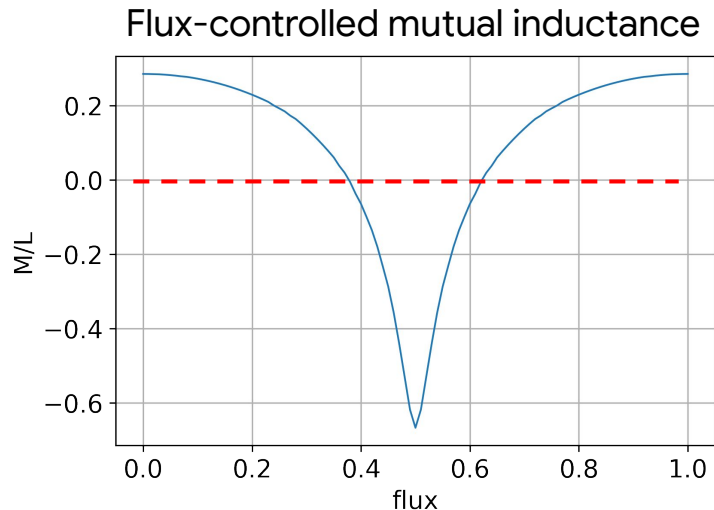
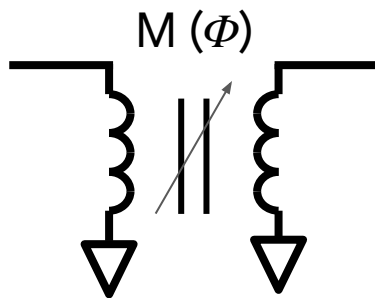
$$\frac{\Phi_0}{2\pi}\delta_0 + LI_c \sin \delta_0 = \Phi$$



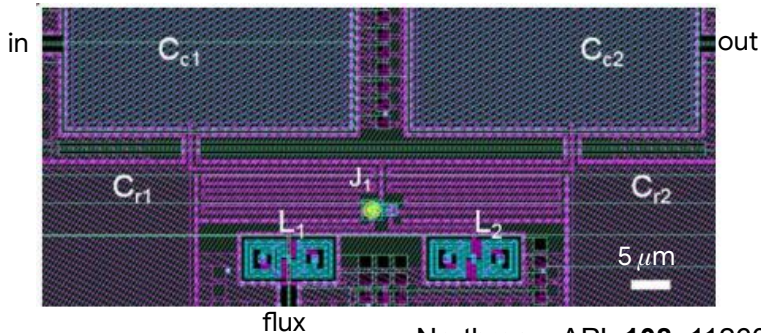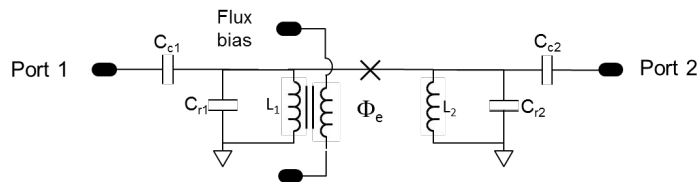
# Microwave Switches for QC

How to implement a microwave switch, if active element necessitates inductive shorts to ground?


- Use junction as tunable coupling
- Embed in band-pass network



Northrop – APL **108**, 112601 (2016)

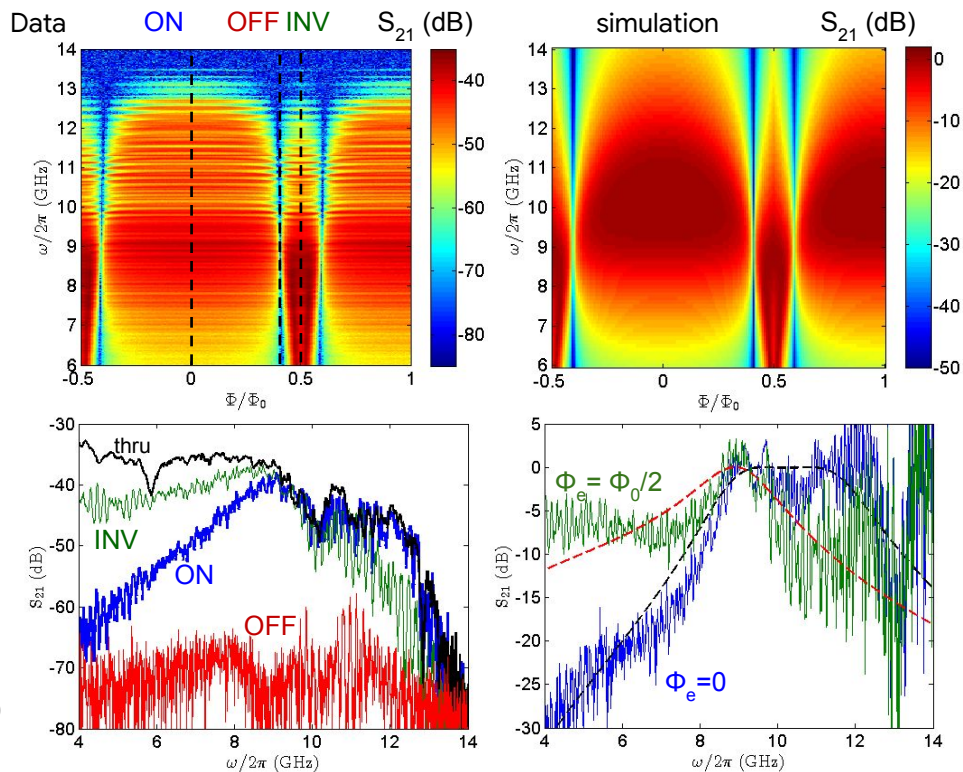


# Microwave Switches for QC

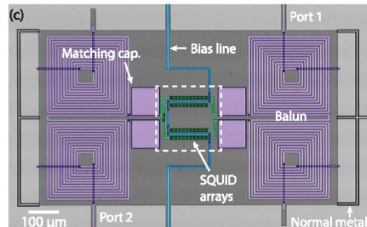


Single-Pole Single Throw (SPST)

JILA – APL **108**, 222602 (2016)

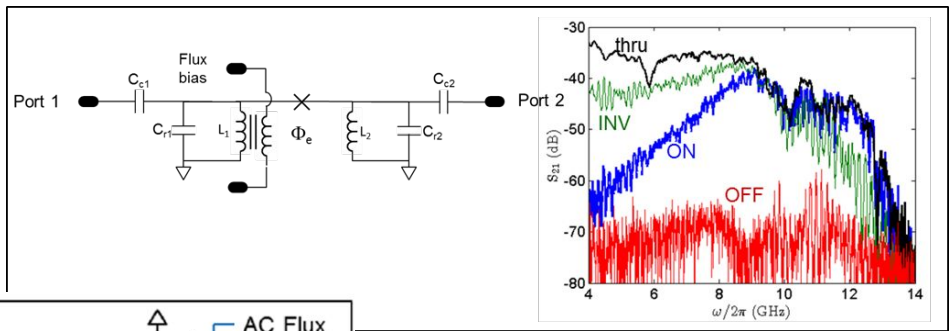


Northrop – APL **108**, 112601 (2016)

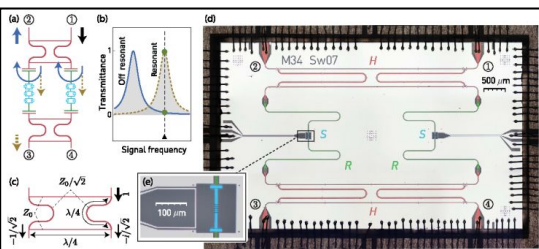


Single-Pole Double Throw (SPDT)

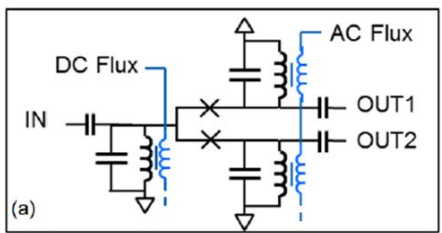ETH – Phys. Rev. Applied **6**, 024009 (2016)



Double-Pole Double Throw (DPDT) transfer


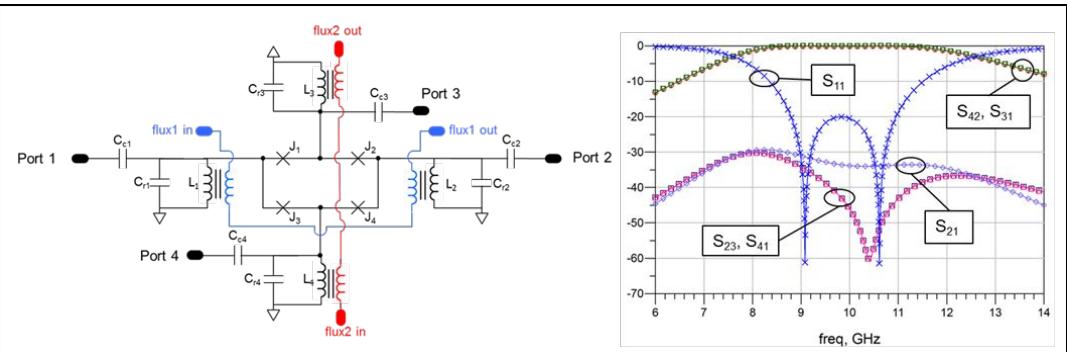


- ✓ Fast
- ✓ Non dissipative
- ✓ GHz bandwidth
- ✓ Flux control


# Mixers and Modulators - Control Pulse Shaping

Analog signal processing with a  
Josephson double-balanced mixer

- Wide-band, no dissipation on chip

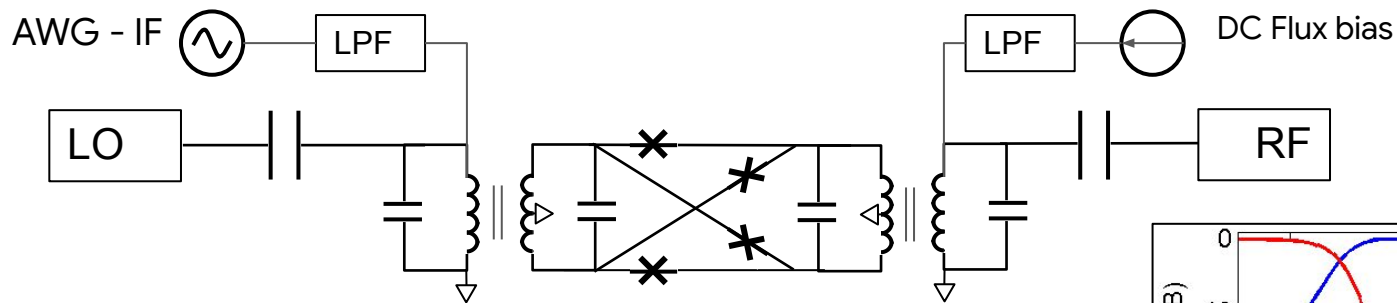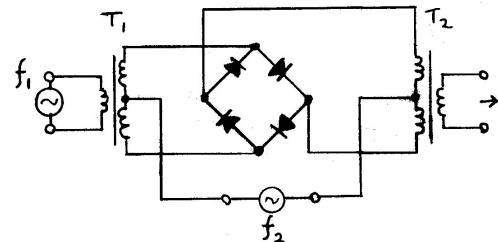



Northrop, JAP **121**, 073904 (2017)

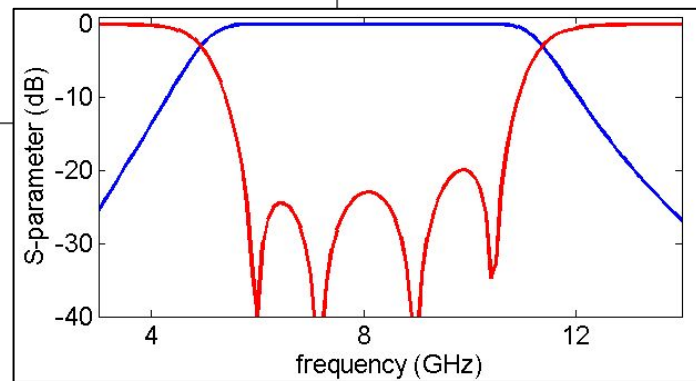


# Mixers and Modulators - Control Pulse Shaping

Analog signal processing with a  
Josephson double-balanced mixer

- Wide-band, no dissipation on chip

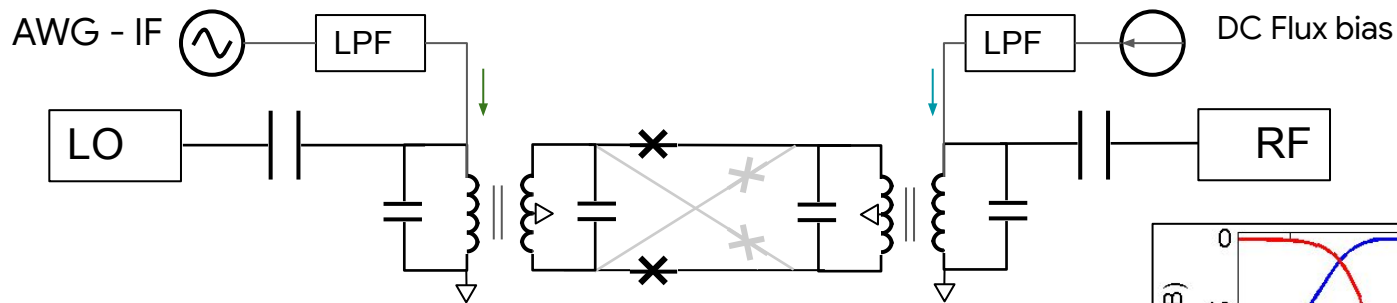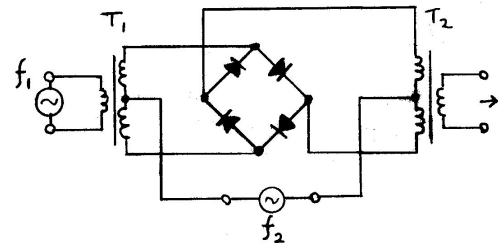

Northrop, JAP **121**, 073904 (2017)


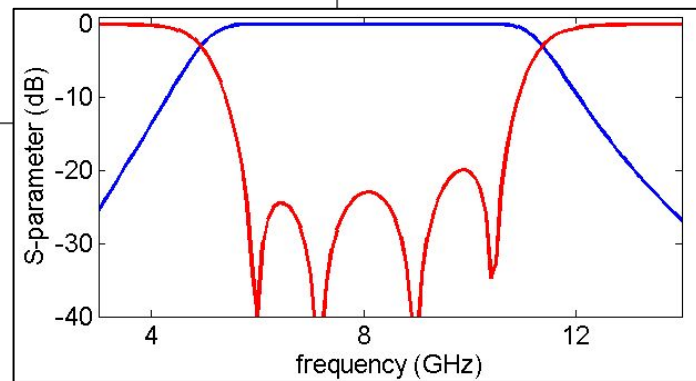





# Mixers and Modulators - Control Pulse Shaping

Analog signal processing with a  
Josephson double-balanced mixer





- Wide-band, no dissipation on chip

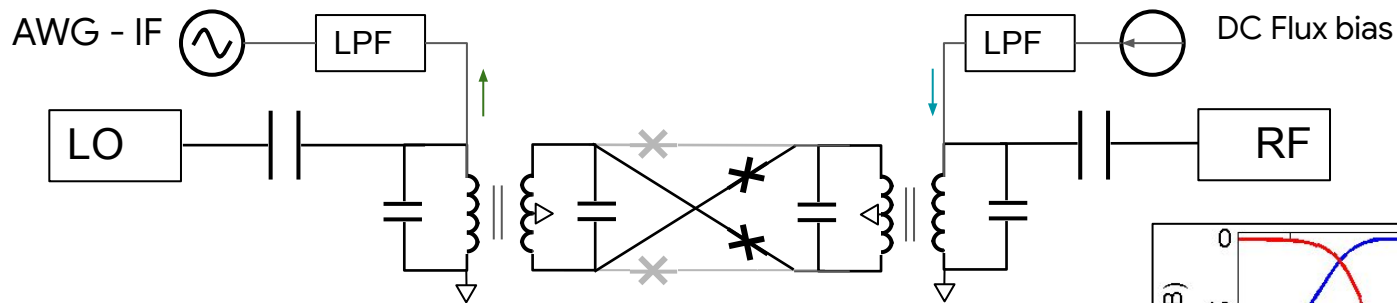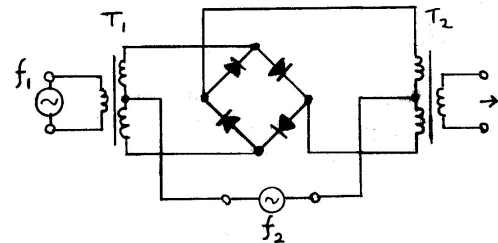


Northrop, JAP **121**, 073904 (2017)

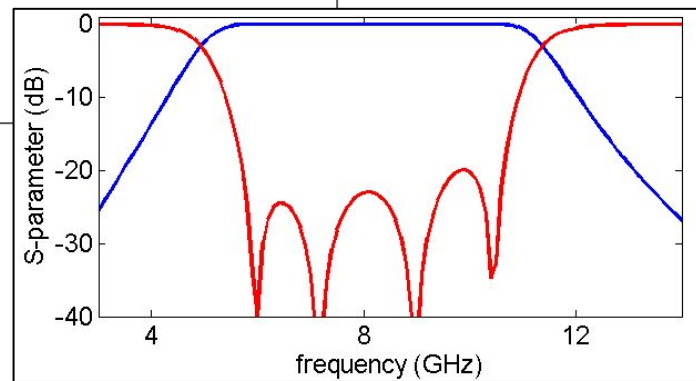
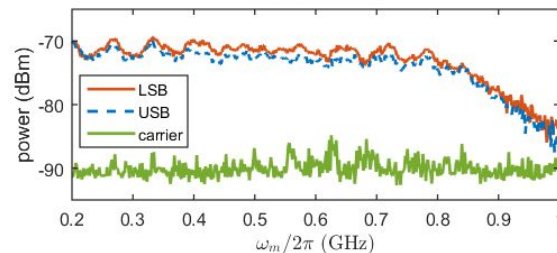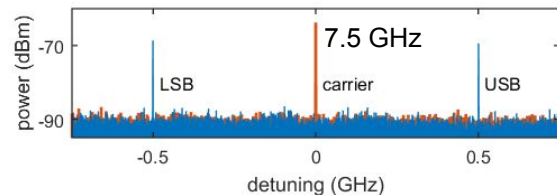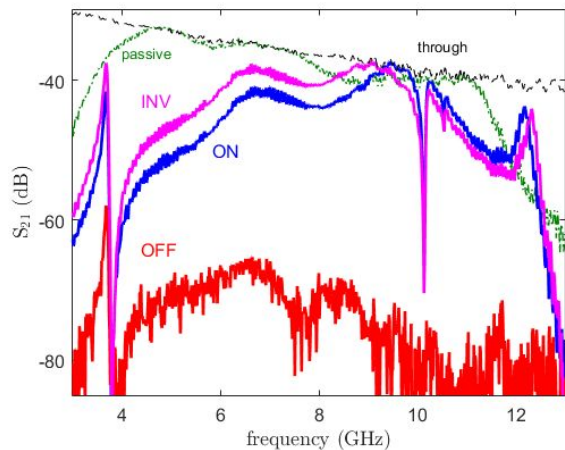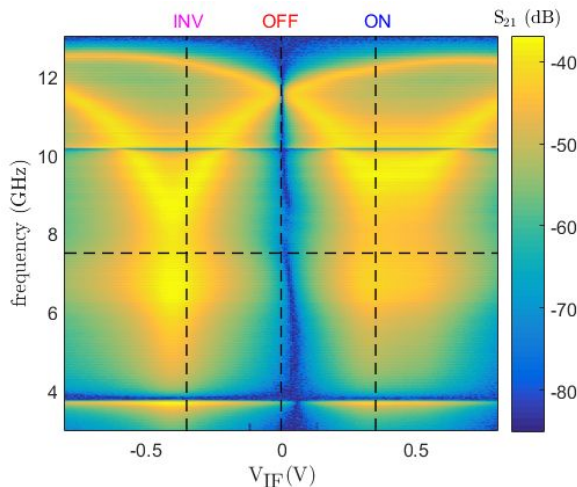
# Mixers and Modulators - Control Pulse Shaping



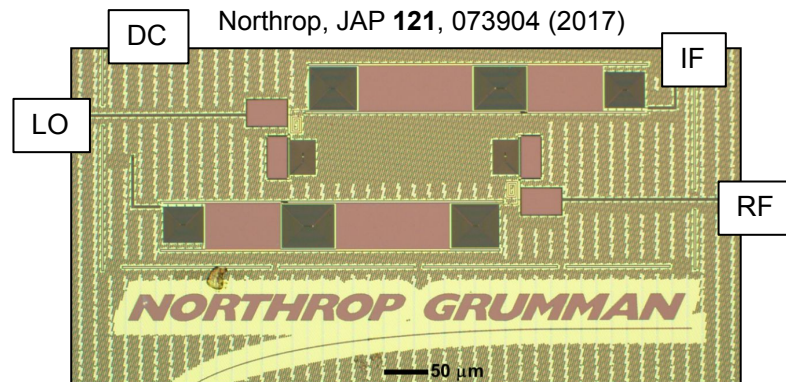- Use Josephson junctions for tunable coupling
  - Non-dissipative operation
- Embed in band-pass network
  - Deal with shunt inductors, ideally low IL, engineer bandwidth
- SQUID design is important
  - Manage nonlinearity, saturation  $> 1$  nW



# Active Superconducting Devices

Needed for qubit readout - amplification & isolation

Signal powers -130 dBm to -120 dBm per qubit

- AC powered
- Josephson junction active elements
- Easy to modulate reactance
- Use parametric amplification and frequency conversion processes
  - Josephson parametric amplifiers
  - Traveling wave parametric amplifiers (next talk!)
  - Parametric circulators
  - Synthetic circulation
- Challenges - bandwidth and saturation power



many circulators


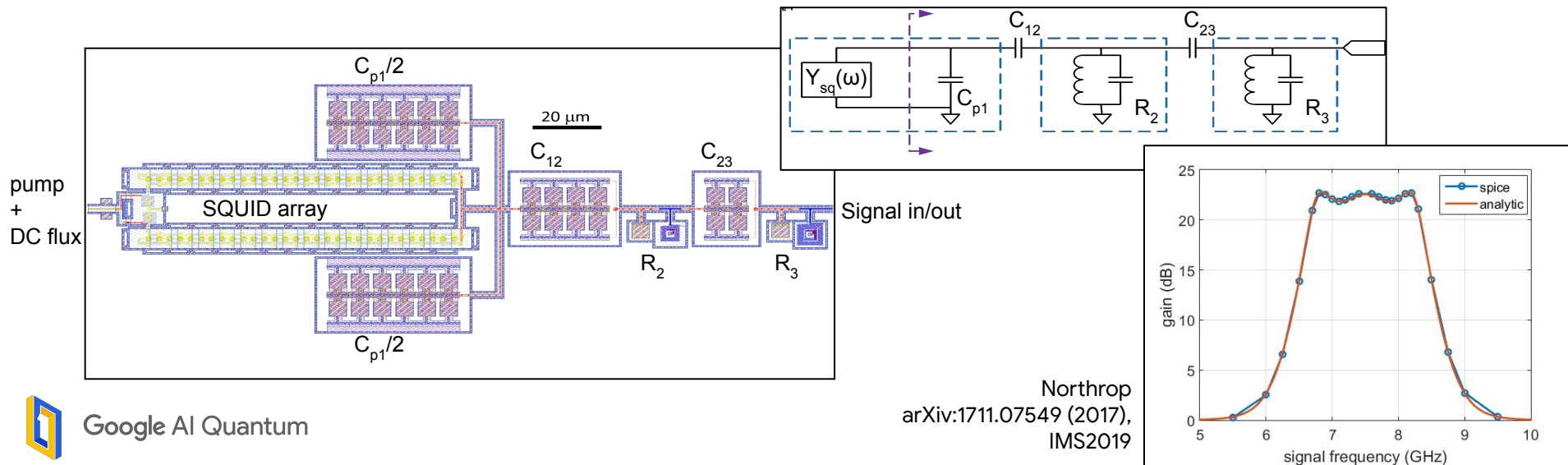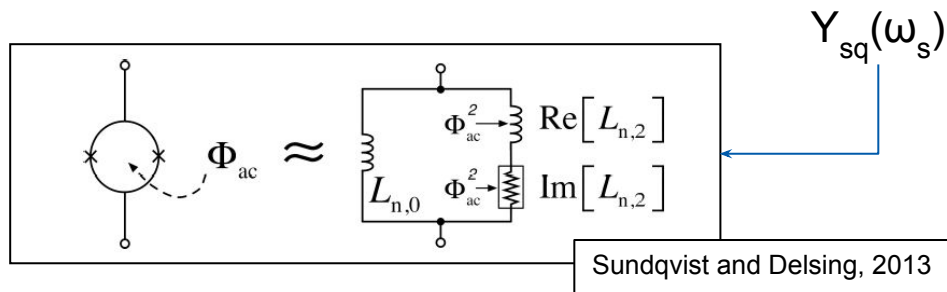
# Josephson Parametric Amplifiers

Pump SQUID at twice the signal frequency  
Effective admittance has **negative real** part




- Band-pass network for impedance match
- SQUID array design for better saturation
- Wide-band reflection gain



# Josephson Parametric Amplifiers
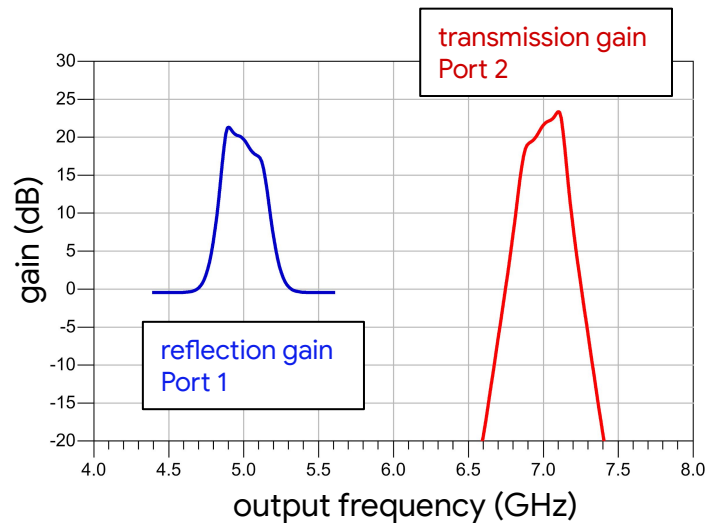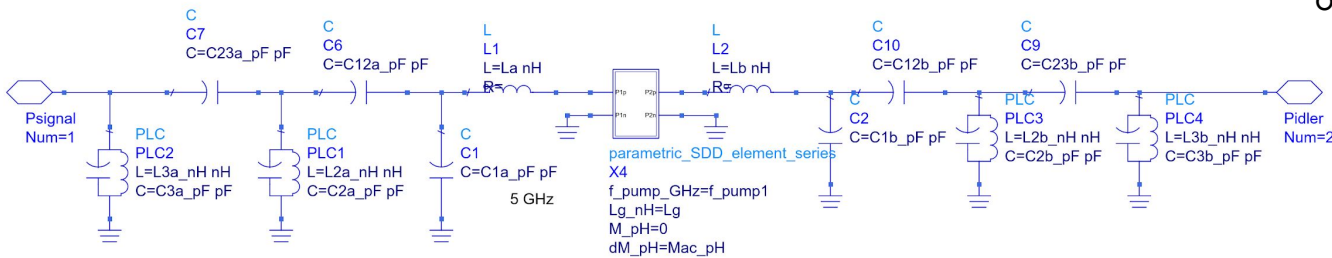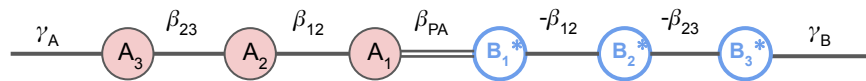
## Non-degenerate matched JPA

- Transmission gain
- Frequency converting
- Automated design via filter synthesis methods







# Synthetic and Parametric Circulators
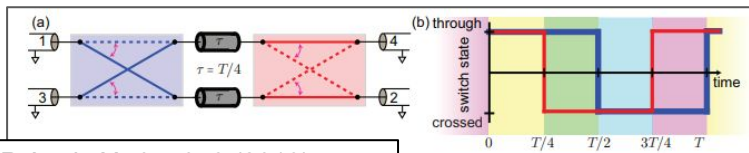
## Synthetic circulation

- 2x IQ mixers (or H-bridges) + delay lines
- Low insertion loss, wide band




JILA, PR Appl. **11**, 044048 (2019)

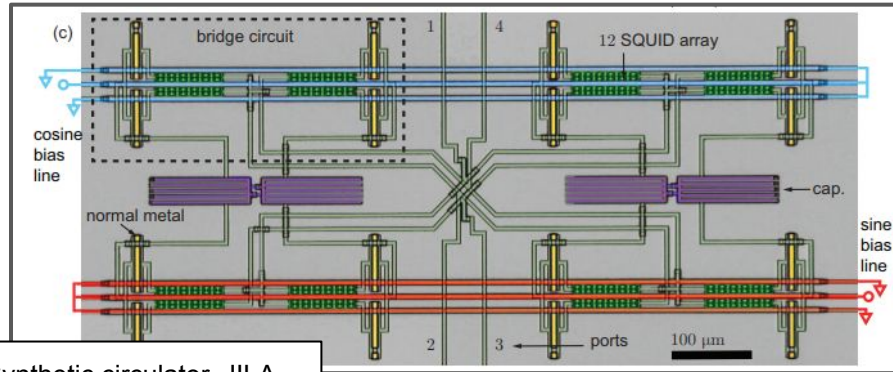

Synthetic circulator, JILA PRX. **7**, 041403 (2017)
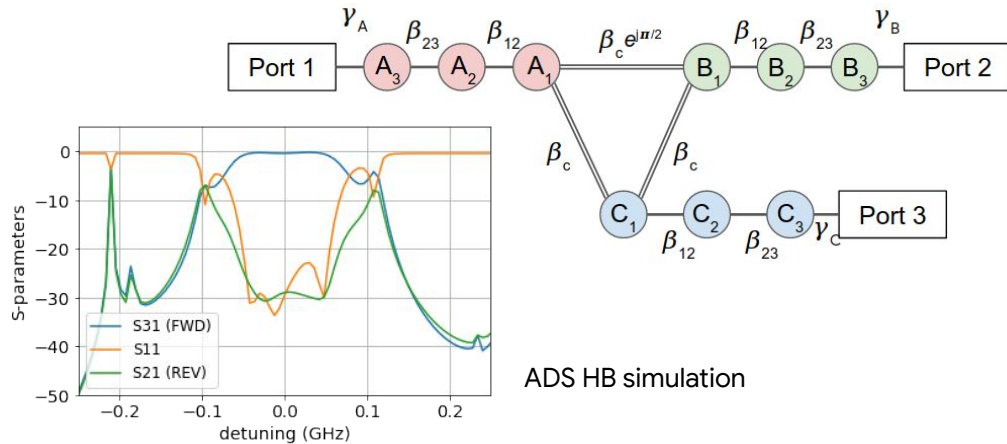
## Parametric circulation

- Parametric conversion
- 3 resonant modes share SQUID
- Bandpass matching network



ADS HB simulation



# Conclusion

- Superconducting IC's complement cryo CMOS for qubit control
  - Low power dissipation means we can integrate on the mix-plate
    - Simplify IO requirements
    - Good for signal integrity
  - Low loss superconducting wiring - more compact, efficient passives. Good for microwaves.
- Unique aspects of superconducting IC design
  - Transformers work down to DC
  - No good “open circuit”
  - Typical circuits present low impedance inductive shunts
  - Flux traps
- Low power microwave and mixed-signal devices
  - Switches and modulators
  - Amplifiers and circulators

